
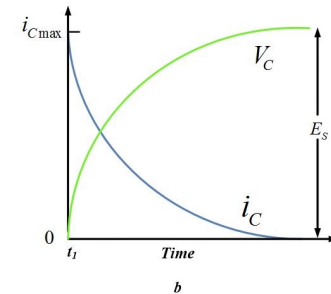


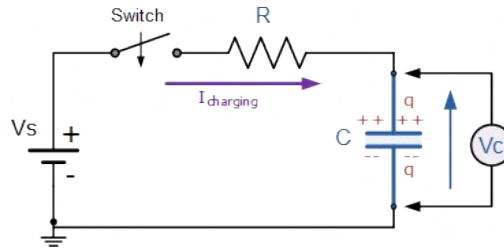

Logo credits go to Moses Won

Discussion 2B

Differential Equations & RC Circuits



Differential Equations

What are they?

- A differential equation relates a function $x(t)$ and its derivatives.

Examples:

- $\frac{dx}{dt} = \lambda x$
- $x' + 4x = \cos t$
- $x'' + 6x' + 9x = \sin x$
- $x'(t) = 4x(t) + 7$
- $x'' + 6x' + 9x = 0$
- $\frac{d}{dt} \vec{x} = A\vec{x} + \vec{b}$
- $\frac{\partial Q}{\partial t} = c_p \frac{\partial y}{\partial t}$

The Solution:

- The **solution** of a differential equation is a function $x(t)$ such that the equation is true for all values of t .

Differential Equations

First Order Differential Equations

- A **first order** differential equation only involves a function $x(t)$ and its first derivative $x'(t)$.

Examples:

$$\frac{dx}{dt} = \lambda x \quad , \quad \frac{dx}{dt} = ax + b \quad , \quad \frac{dx}{dt} + ax = f(t)$$

Initial Conditions

- The **initial conditions** of a differential equation lets us solve for a particular instance of the solution.

$$x(0) = x_0 \quad \leftarrow \text{some constant}$$

rential equation $d^2s/dt^2 = -32$ becomes
denoted by a **subscript notation** indic
ple, with the subscript notation the

Order The order of a differential equation is the highest derivative in the equation. For

second order \downarrow \downarrow first order

$$\frac{d^2y}{dx^2} + 5\left(\frac{dy}{dx}\right)^3 - 4y = e^x$$

ry differential equation. In Example 1,
t-order ODEs, whereas in (3) the first

first order

3



TRIGGERED

Two Important Examples

- $x'(t) = 3x(t); x(0) = 5$

$\lambda = 3$, guess $x = Ke^{3t}$

$$x(t=0) = Ke^{3 \cdot 0} = Ke^0 = K = 5$$

$$x = 5e^{3t}$$

- $x'(t) = -2x(t) + 4; x(0) = 3$

Know: $-2K_1 e^{-2t} = -2K_1 e^{-2t} - 2K_2 + 4$

$$0 = -2K_2 + 4 \rightarrow K_2 = 2$$

$$x(t) = K_1 e^{-2t} + 2$$

$$x(t=0) = K_1 + 2 = 3 \rightarrow K_1 = 1$$

$$x(t) = e^{-2t} + 2$$

$$\frac{dx}{dt} = \lambda x; x(0) = x_0$$

Guess: $x(t) = Ke^{\lambda t}$ ← arbitrary constant

Check: $x'(t) = K\lambda e^{\lambda t}$
 $= \lambda Ke^{\lambda t}$
 $= \lambda \cdot x(t)$

$$\frac{dx}{dt} = \lambda x + u; x(0) = x_0$$

Try: $\lambda \cancel{Ke^{\lambda t}} = \lambda \cancel{K} e^{\lambda t} + u$

$$0 = u$$

contradiction!

Guess: $x(t) = K_1 e^{-2t} + K_2$

$$x'(t) = -2x + 4$$

$$x'(t) = -2K_1 e^{-2t}$$

$$-2x + 4 = -2(K_1 e^{-2t} + K_2) + 4$$

$$= -2K_1 e^{-2t} - 2K_2 + 4$$

Common Solutions

Let's take a look at the first order differential equation: $\mathbf{x}'(t) + \mathbf{a} \mathbf{x}(t) = \mathbf{b}$
diff from $x' = \lambda x + u$

- If $b = 0$, this is called a **homogeneous** differential equation.

- Given $x(0) = k$, the solution is $x(t) = k e^{-at}$

Guess $x(t) = A e^{\lambda t}$

$$A = k$$

$$x(0) = k$$

$$x(t) = x(0) e^{-at}$$

- If $b \neq 0$, this is called a **non-homogeneous** differential equation.

- Given $x(0) = k$, the solution is $x(t) = x(0) e^{-at} - \frac{b}{a} (e^{-at} - 1)$

Guess: $x(t) = A e^{\lambda t} + B$

$$= \underbrace{\left(x(0) - \frac{b}{a}\right)}_A e^{-at} + \underbrace{\frac{b}{a}}_B$$

Uniqueness

Given a first order differential equation: $\mathbf{x}'(t) + \mathbf{a} \mathbf{x}(t) = \mathbf{b}$

- If we are given an initial condition $x(0) = k$, then there will always be a unique solution $x(t)$
$$= \left(x(0) - \frac{b}{a} \right) e^{-at} + \frac{b}{a}$$
- The proof is hard, and we took it out of the HW for this sem.
- When your solution isn't unique ->



1 RC Circuits

In this problem, we will be using differential equations to find the voltage across a capacitor over time in an RC circuit. We set up our problem by first defining three functions over time: $I(t)$ is the current at time t , $V(t)$ is the voltage across the circuit at time t , and $V_C(t)$ is the voltage across the capacitor at time t .

Recall from 16A that the voltage across a resistor is defined as $V_R = RI_R$ where I_R is the current across the resistor. Also, recall that the voltage across a capacitor is defined as $V_C = \frac{Q}{C}$ where Q is the charge across the capacitor.

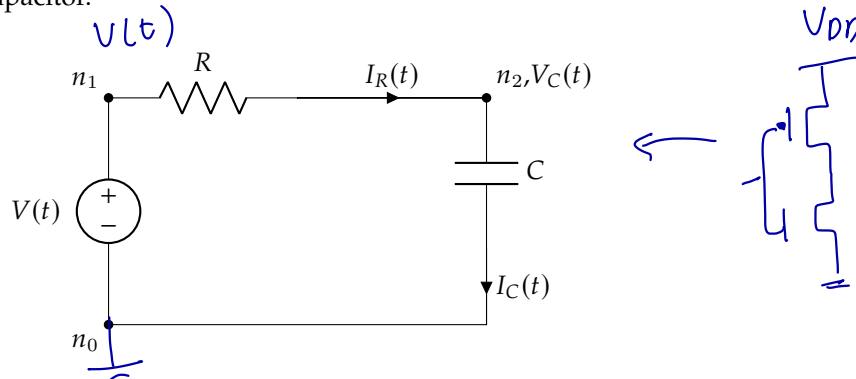


Figure 1: Example Circuit

- a) First, find an equation that relates the current through the capacitor $I_C(t)$ with the voltage across the capacitor $V_C(t)$.

Know: $Q = C \cdot V_C$, $I = \frac{dQ}{dt}$

$$\frac{dQ}{dt} = C \frac{dV_C}{dt} \rightarrow I_C = C \frac{dV_C}{dt}$$

- b) Using nodal analysis, write a differential equation for the capacitor voltage $V_C(t)$. Note that this is also the voltage for the node n_2 .

1. Identify Nodes

Done.

2. Write KCL

$$I_R = I_C$$

3. I/V Relations

$$I_R = \frac{V(t) - V_C(t)}{R} = C \frac{dV_C}{dt} = I_C$$

$$C \frac{dV_C}{dt} = -\frac{1}{R} V_C(t) + \frac{V(t)}{R}$$

4. Simplify

$$\frac{dV_C}{dt} + \frac{1}{RC} V_C(t) = \frac{V(t)}{RC}$$

- c) Let's suppose that at $t = 0$, the capacitor is charged to a voltage V_{DD} ($V_C(0) = V_{DD}$). Let's also assume that $V(t) = 0$ for all $t \geq 0$.

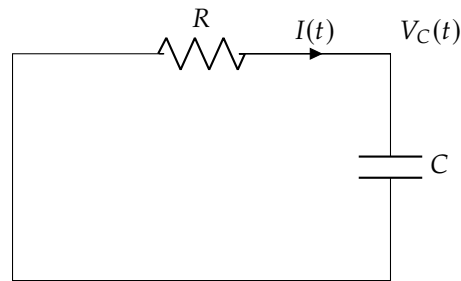


Figure 2: Circuit for part (d)

$$V_C(0) = V_{DD}$$

$$V(t) = 0 \text{ for all } t \geq 0$$

Solve the differential equation for $V_C(t)$ for $t \geq 0$.

Know: $\frac{dV_C}{dt} + \underbrace{\frac{1}{RC}}_a V_C(t) = \frac{V(t)}{RC} = 0$ $b = 0$

$$V_C(0) = V_{DD}$$

Given $\frac{dx}{dt} + ax = 0$

$$X(t) = X(0)e^{-at}$$

Plugging in $a = \frac{1}{RC}$, $X(0) = V_{DD}$, we see that

$$V_C(t) = V_{DD} e^{-\frac{1}{RC} \cdot t}$$

- d) Now, let's suppose that we start with an uncharged capacitor $V_C(0) = 0$. We apply some constant voltage $V(t) = V_{DD}$ across the circuit. Solve the differential equation for $V_C(t)$ for $t \geq 0$.

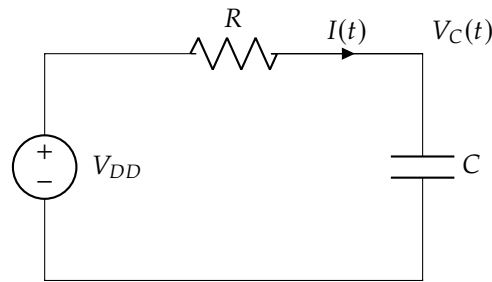


Figure 3: Circuit for part (e)

$$V(t) = V_{DD} \text{ for all } t$$

$$\frac{dV_C}{dt} + \underbrace{\frac{1}{RC}}_a V_C(t) = \frac{V(t)}{RC} = \underbrace{\frac{V_{DD}}{RC}}_b \quad V_C(0) = 0$$

$$\begin{aligned} x(t) &= \left(x(0) - \frac{b}{a} \right) e^{-at} + \frac{b}{a} \\ &= x(0) e^{-at} - \frac{b}{a} (e^{-at} - 1) \\ &= (0) \cdot e^{-\frac{1}{RC}t} - \frac{\frac{V_{DD}}{RC}}{\frac{1}{RC}} (e^{-\frac{1}{RC}t} - 1) \\ &= 0 - V_{DD} (e^{-t/RC} - 1) \\ &= V_{DD} (1 - e^{-t/RC}) \end{aligned}$$

Note: There's an alternate method to solving diff-egs called substitution of vars.

- d) Now, let's suppose that we start with an uncharged capacitor $V_C(0) = 0$. We apply some constant voltage $V(t) = V_{DD}$ across the circuit. Solve the differential equation for $V_C(t)$ for $t \geq 0$.

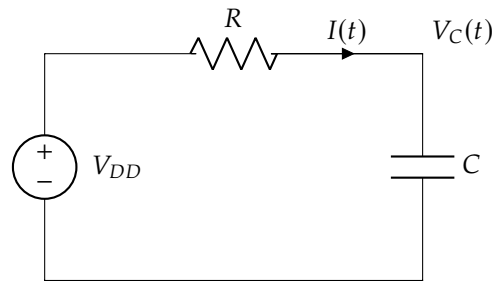


Figure 3: Circuit for part (e)

Alternate Sol:

$$\frac{dV_C}{dt} = -\frac{1}{RC} V_C + \frac{V_{DD}}{RC}$$

$$V_C(0) = 0$$

Define a new variable

$$x = V_C - V_{DD}$$

Then

$$\frac{dx}{dt} = \frac{dV_C}{dt}$$

since V_{DD} is constant

and
plug in x

$$-\frac{1}{RC} x = -\frac{1}{RC} (V_C - V_{DD})$$

This means $\frac{dV_C}{dt} = -\frac{1}{RC} V_C + \frac{V_{DD}}{RC}$ can be rewritten as

$$\frac{dx}{dt} = -\frac{1}{RC} x \quad \text{This has solution } x(t) = x(0) e^{-\frac{1}{RC} t}$$

$$x(0) = V_C(0) - V_{DD} = -V_{DD} \quad \text{so } x(t) = -V_{DD} e^{-t/RC}$$

Lastly change variables back to V_C .

$$V_C = x + V_{DD} = V_{DD} - V_{DD} e^{-t/RC}$$

2 Graphing RC Responses

Consider the following RC Circuit with a single resistor R , capacitor C , and voltage source $V(t)$.


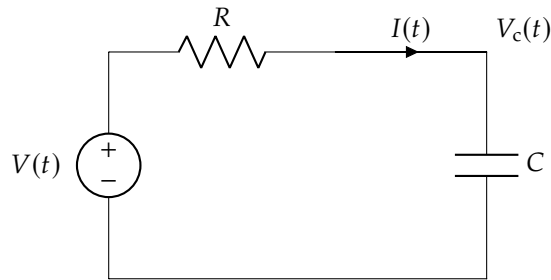


Figure 4: Example Circuit

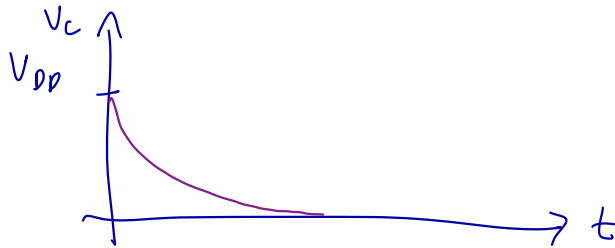- a) Let's suppose that at $t = 0$, the capacitor is charged to a voltage V_{DD} ($V_c(0) = V_{DD}$) and that $V(t) = 0$ for all $t \geq 0$. Plot the response $V_c(t)$.

Recall that $V_c(t) = V_{DD} e^{-\frac{1}{RC} t}$


We can plot this on a graphing calculator



- b) Now let's suppose that at $t = 0$, the capacitor is uncharged ($V_c(0) = 0$) and that $V(t) = V_{DD}$ for all $t \geq 0$. Plot the response $V_c(t)$.

Recall that $V_c(t) = V_{DD} (1 - e^{-\frac{1}{RC} t})$.

The plot is shown below

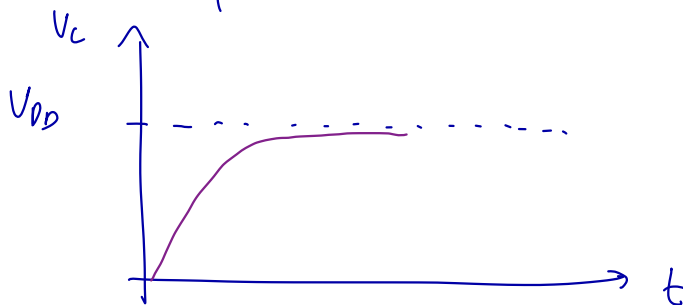

To better understand our responses, we now define a **time constant** which is a measure of how long it takes for the capacitor to charge or discharge. Mathematically, we define τ as the time at which $V_C(\tau)$ is $\frac{1}{e} = 36.8\%$ away from its steady state value.

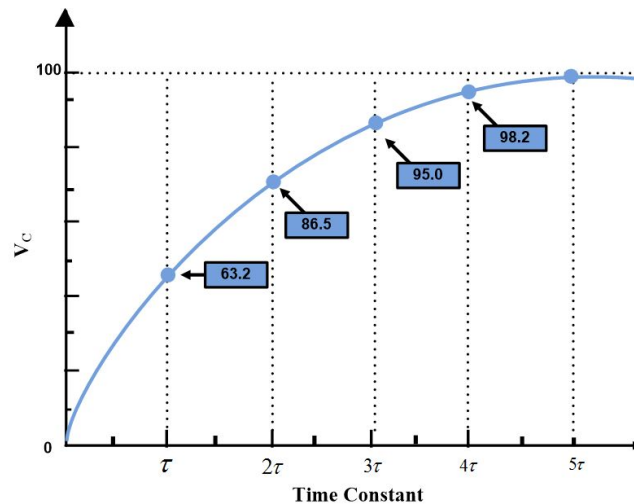


Figure 5: Different values of capacitor voltage at different times, relative to τ .

- c) Suppose that $V_{DD} = 5\text{ V}$, $R = 100\ \Omega$, and $C = 10\ \mu\text{F}$. What is the time constant τ for this circuit?

Let's take the discharging case from part (a).

By definition τ is the time at which $V_C(\tau) = \frac{V_{DD}}{e}$.

We can solve for τ as follows:

$$V_C(\tau) = V_{DD} e^{-\tau/RC} = \frac{V_{DD}}{e}$$

$$e^{-\tau/RC} = \frac{1}{e}$$

$$-\tau/RC = \ln\left(\frac{1}{e}\right) = -1 \rightarrow \tau = RC = 1\text{ ms}$$

or 0.001 s.

- d) Going back to part (b), on what order of magnitude of time (nanoseconds, milliseconds, 10's of seconds, etc.) does this circuit settle (V_C is $> 95\%$ of its value as $t \rightarrow \infty$)?


Looking at the graph above, it will take 3τ to reach 95% of the steady state value.

Since $\tau = RC = 1\text{ ms}$, it will take 3 ms to reach within $0.95 V_{DD}$.

- e) Give 2 ways to reduce the settling time of the circuit if we are allowed to change one component in the circuit.


$\tau = RC$. To reduce the time constant, we should either decrease R or decrease C .

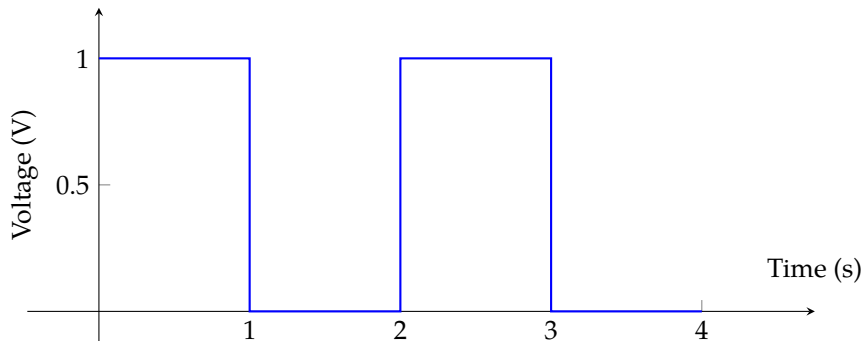- f) Suppose we have a source $V(t)$ that alternates between 0 and $V_{DD} = 1$ V. Given $RC = 0.1$ s, plot the response V_c if $V_c(0) = 0$.



$V(t)$ alternates between 1 and 0. However, it stays constant from $[0, 1)$, $[1, 2)$, ... Therefore, we can solve the differential equations assume $V(t)$ is constant over an interval.

Plot will look like this

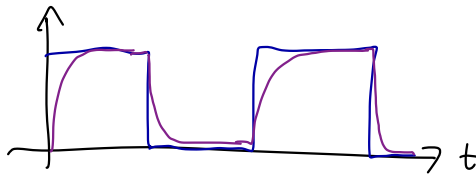

Note that $\tau = 0.1$ s and we wait 10τ before switching $V(t)$.

- g) Now suppose we have the same source $V(t)$ but $RC = 1$ s, plot the response V_c if $V_c(0) = 0$.

Here $\tau = 1$ s meaning after 1 s we will only reach 63% of V_{DD} . Note that $63\% = 1 - \frac{1}{e}$.

